

# Miniature Programmable Power Supply

**EE 344: ELECTRONIC DESIGN LAB**

## Project Report

by

**Abhishek M, Gouri S Dev, G Srilasya Sasidhar**  
(Roll Numbers: 200070003, 200070019, 200070022)

**Group : TUES-33**

Faculty Mentors

**Prof. Joseph John, Prof. Shiladri Chakraborty**



Department of Electrical Engineering  
Indian Institute of Technology Bombay  
April 2023


# Contents

|           |                                       |           |
|-----------|---------------------------------------|-----------|
| <b>1</b>  | <b>Introduction</b>                   | <b>3</b>  |
| 1.1       | Project Goals . . . . .               | 3         |
| <b>2</b>  | <b>Block Diagram</b>                  | <b>4</b>  |
| 2.1       | Block Diagram explained: . . . . .    | 5         |
| <b>3</b>  | <b>Schematic</b>                      | <b>6</b>  |
| 3.1       | Component Selection Details . . . . . | 7         |
| <b>4</b>  | <b>PCB layout</b>                     | <b>8</b>  |
| 4.1       | Top Layer . . . . .                   | 9         |
| 4.2       | Bottom Layer . . . . .                | 10        |
| <b>5</b>  | <b>CAD Model</b>                      | <b>11</b> |
| <b>6</b>  | <b>Subsystem Test Results</b>         | <b>12</b> |
| 6.1       | Boost Circuit . . . . .               | 12        |
| 6.1.1     | Test Setup . . . . .                  | 12        |
| 6.1.2     | Methodology . . . . .                 | 12        |
| 6.1.3     | Result . . . . .                      | 13        |
| 6.2       | Digipot . . . . .                     | 13        |
| 6.2.1     | Test Circuit . . . . .                | 13        |
| 6.2.2     | Methodology . . . . .                 | 13        |
| 6.2.3     | Results . . . . .                     | 13        |
| 6.2.4     | Code . . . . .                        | 14        |
| 6.3       | ADC . . . . .                         | 15        |
| 6.3.1     | Test Circuit . . . . .                | 15        |
| 6.3.2     | Methodology . . . . .                 | 15        |
| 6.3.3     | Results . . . . .                     | 15        |
| 6.3.4     | Code . . . . .                        | 15        |
| <b>7</b>  | <b>Final Testing</b>                  | <b>17</b> |
| 7.1       | Code for the full system . . . . .    | 17        |
| <b>8</b>  | <b>Components BOM</b>                 | <b>21</b> |
| <b>9</b>  | <b>Major Problems Faced</b>           | <b>21</b> |
| <b>10</b> | <b>Future Work</b>                    | <b>22</b> |
 
# 1 Introduction

It is quite difficult to transfer the benchtop power supply that is provided in the WEL lab when using it for different experiments. We lack a dependable power source that is compact, adaptable, and able to generate a range of voltages from a single input supply for many portable projects.

A power supply that can draw power from the AC mains using the standard C-type mobile charger (5V), and generate a stepped-up range of voltages using the charger's DC voltage could be quite useful in this scenario, and the aim of this project is to build one such miniature programmable power supply.



Miniature Programmable Power Supply

## 1.1 Project Goals


In this project, we have made a programmable compact power supply with the following specifications for input and output:

Input: 5V via USB-C of a regular mobile phone charger.

Output: 12V to 15V

Users can easily set the desired output voltage with the help of push buttons and a toggle switch. The output voltage can be conveniently plugged into a breadboard and will be immediately displayed on an LCD display

## 2 Block Diagram

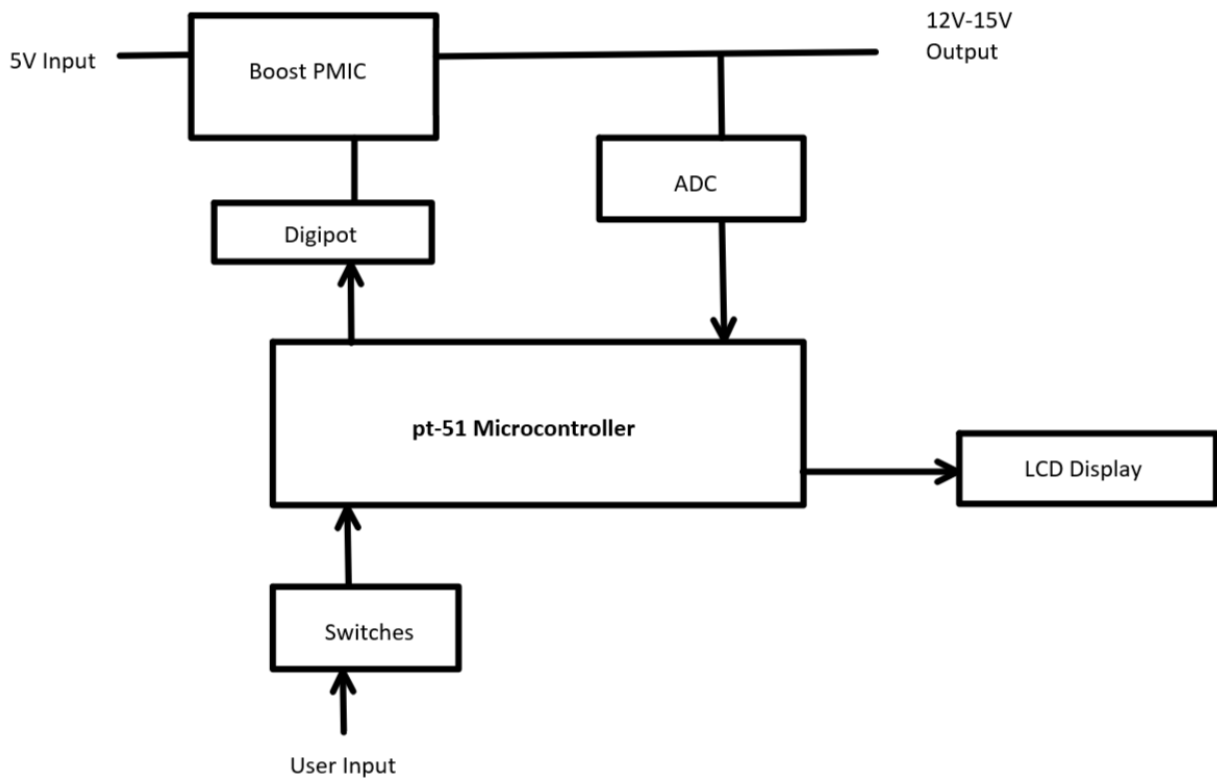

Block Diagram


The miniature portable power supply is composed of the following:

- Input port for a 5V supply
- Buttons: Means to take input from the user.
- Boost Converter: The DC-DC converter will step up the input 5V to a voltage in the range of 12V to 15V depending upon the input given by the user through the buttons.
- Analog-to-Digital Converter: Converts the analog output voltage signal to a 10-bit digital value.
- LCD Display: A display to show the user the present voltage output.
- Microcontroller: It takes the input from the user (the required voltage value) and uses it to change the output voltage accordingly. It also takes the output of the ADC and displays the output voltage on the LCD.

## 2.1 Block Diagram explained:

- The user sets the output voltage required using two push buttons and a toggle switch. The toggle switch is used to switch between coarse and fine voltage adjustment, while the push buttons are used to increase and decrease the output voltage.
- The boost PMIC receives a 5V supply from the USB-C charger. It then boosts the voltage and its output voltage is controlled by its feedback resistors. Since we need a variable  $V_{out}$ , we use a digipot as a variable resistor in place of one of the feedback resistors and thereby vary the value of  $V_{out}$  as per the input given by the user through the switches.  $V_{out} = (\frac{R_{digipot}}{R_1} + 1)1.255$ , where  $R_1$  is the non-varying feedback resistance.
- To control the resistance of the digipot we have used the pt-51 microcontroller. Once the user inputs a value through the rocker switch and push buttons, the pt-51 microcontroller adjusts the input passed to the digipot, thereby altering its resistance accordingly.
- The resulting output voltage is then directed to a 10-bit ADC which converts the voltage to a digital value. This 10-bit digital value is then passed to the microcontroller, which displays it on the LCD in real time.

### 3 Schematic

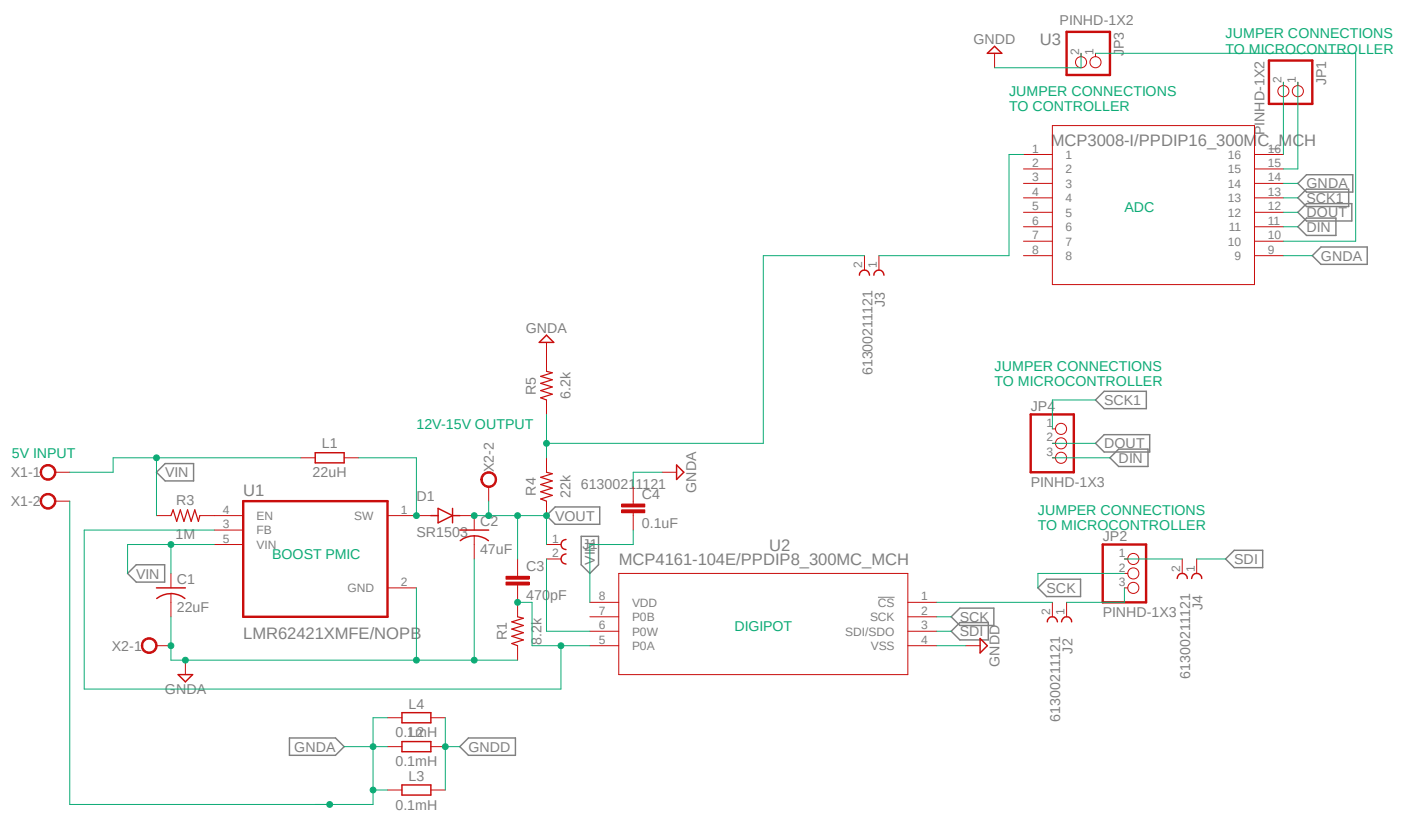

### 3.1 Component Selection Details

Following are the values of the passives in the boost circuit, chosen as per the datasheet:

$$R_1 = 12k\Omega$$

$$R_3 = 1M\Omega$$

$$C_1 = 22\mu F$$

$$C_2 = 4.7\mu F$$

$$C_3 = 470pF$$


Calculation of Inductance for the boost circuit:

$$f_{sw} = 1.6MHz$$

$$\Delta i_L = 0.2 * i_L \text{ (limiting ripple current to 20 percentage)}$$


$$L_1 = \frac{V_{in} * D * T_s}{(2\Delta i_L)} = 16 \mu H$$

## 4 PCB layout

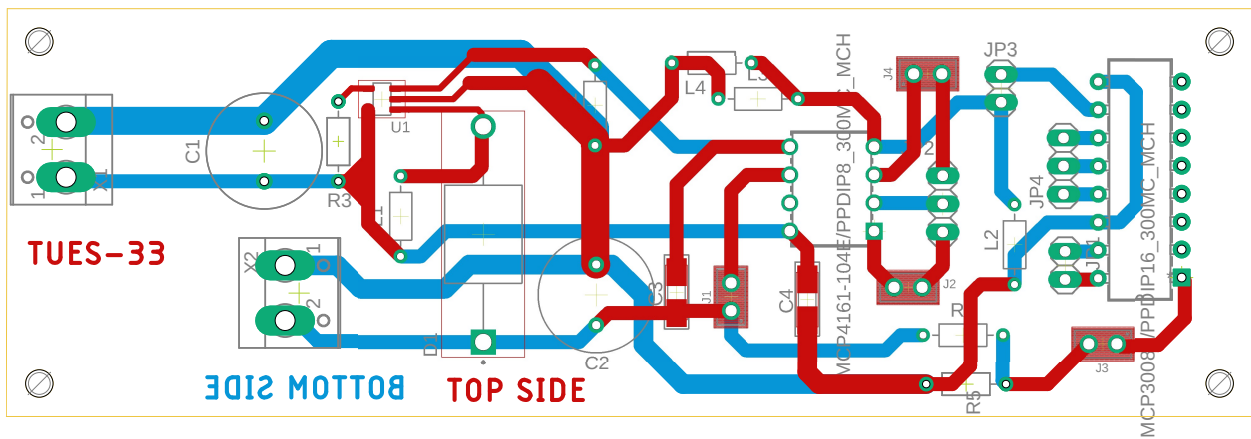





## 4.1 Top Layer

 

## 4.2 Bottom Layer

 

## 5 CAD Model

 


- The miniature programmable power supply will be enclosed in the box. The left bottom face has the cavities for the LCD display (larger rectangular cavity), and the switches. The extrusion will act as a ledge on which the PCB will be placed.
- The top middle face has an extrusion on which the USB-C connector will be placed and the USB-C charger will be connected to it through the cavity right above it.
- The middle bottom face has two holes through which the output wires can be taken and connected to the breadboard for use.


## 6 Subsystem Test Results

### 6.1 Boost Circuit

#### 6.1.1 Test Setup

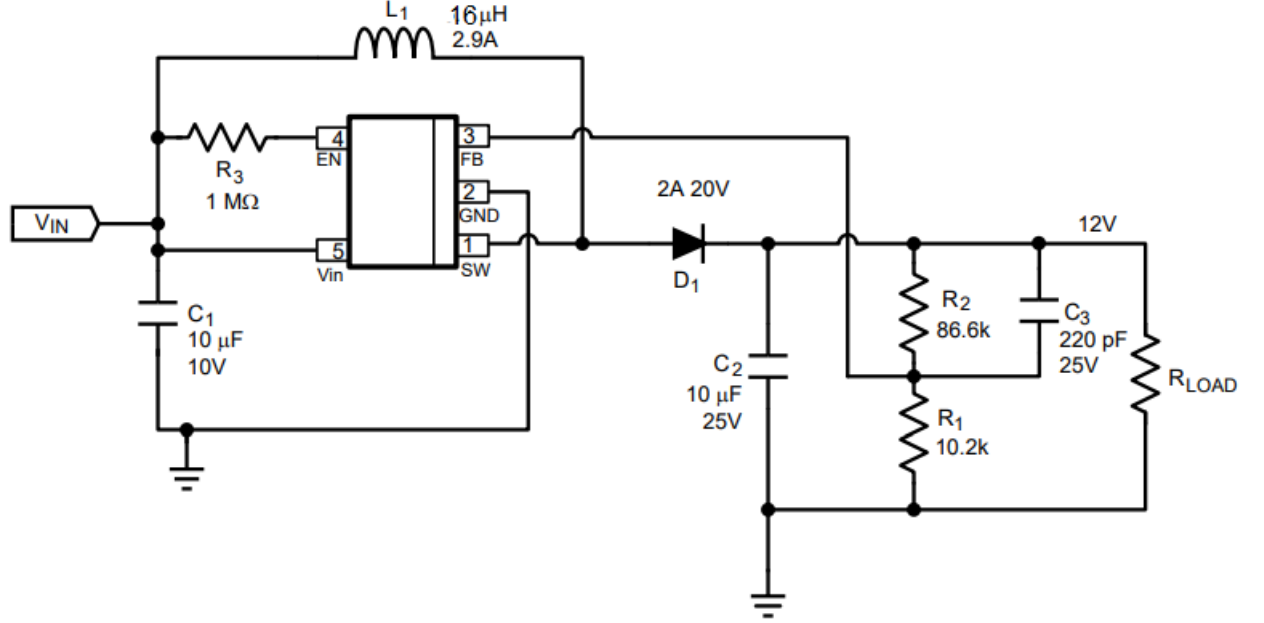

Boost PMIC test setup circuit diagram

 

Test setup for PMIC

#### 6.1.2 Methodology

The boost circuit is made as in the diagram above where the value of  $V_{out}$  and  $R_2$  are related as  $R_2 = ((\frac{V_{out}}{1.255}) - 1)R_1$ . To test its functioning we provided a supply of 5V and

used a potentiometer in place of  $R_2$  (shown in image). The potentiometer resistance was varied continuously and we observed the change in  $V_{out}$  to check whether it was varying according to the relation given above.


### 6.1.3 Result

The output voltage was varying as expected with change in  $R_2$  and therefore we concluded that the PMIC testing is successful and that the boost subsystem is working.

**Link:** Click for Boost subsystem testing video.

## 6.2 Digipot

### 6.2.1 Test Circuit

 

Test connections for Digipot

### 6.2.2 Methodology

For testing the digipot, we make the connections as shown in the above circuit diagram. Here, the resistance between the wiper pin and one of the end terminals of the potentiometer has to be used as the feedback resistance in the boost subsystem to control its output voltage.

For testing, we have varied the input parameter given to the digipot through the toggle switch and push buttons to change its resistance and measured its resistance with a multimeter to see if it is changing as per our expectations.

### 6.2.3 Results

Through this code, we confirmed that the digipot was able to continuously update itself for a given range with the help of SPI communication with pt-51.

The digipot is working successfully as a variable resistor and can be used as a feedback resistor for the boost PMIC.

**Link:** Click for Digipot subsystem testing video.


The change in the resistance between the wiper pin and one of the end terminals of the digipot according to the input given through switches can be seen here.

#### 6.2.4 Code

```
1
2 /*****
3 This is the test for the digipot MCP4161 using the SPI already
   given
4 *****/
5
6 #include <at89c5131.h>
7 #include "digipot.h"
8 #include "spi.h"
9 #include "lcd.h"
10
11 unsigned int resis;
12 unsigned int i;
13
14 void main(void)
15 {
16
17     spi_init();          // initialize SPI interface
18     digipot_init();      // initialize digipot
19
20     for (i = 1; i <150; i = i+4){
21         resis = i;
22         digipot_write(resis);
23         msdelay(100);
24     }
25
26 }
```

## 6.3 ADC

### 6.3.1 Test Circuit

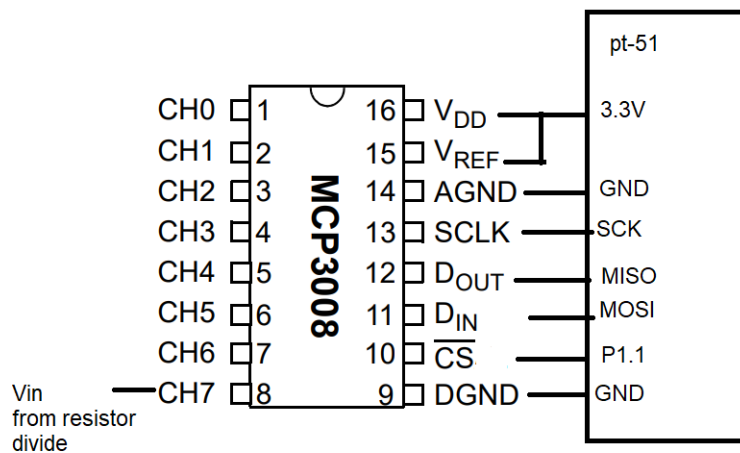

Test connections for ADC

### 6.3.2 Methodology

Since the microcontroller has to display the output voltage on LCD, we have to down convert the 12-15V output of the boost circuit to 0-3.3V using a resistor divider so as to give it as input to the ADC.

To test the ADC, we connect its CH7 channel to the output voltage signal. We then interface the ADC with the microcontroller using SPI. This code takes in the value of the CH7 channel and accurately converts it to its corresponding 10-bit representation. The microcontroller then displays this value on the LED.

### 6.3.3 Results

After running the code, we confirm that the test was successful and that the ADC is functioning as intended.

**Link:** Click for ADC subsystem testing video

### 6.3.4 Code

```
1 /*****
2 This is the code to interface the adc MCP3008 using SPI
3 *****/
4
5 #include <at89c5131.h>
```

```

6 #include "lcd.h"    //Driver for interfacing lcd
7 #include "adc.h"    //Driver for interfacing ADC ic MCP3008
8 #include "spi.h"
9
10 char adc_ip_data_ascii[6] = {0, 0, 0, 0, 0, '\0'};
11 code unsigned char display_msg1[] = "Volt.: ";
12 code unsigned char display_msg2[] = " mV";
13
14 void main(void)
15 {
16     int j = 0;
17     unsigned int adc_data = 0;
18
19     spi_init();
20     adc_init();
21     lcd_init();
22
23     while (1)
24     {
25         unsigned int x;
26         // Read analog value from 7th channel of ADC Ic MCP3008
27         // Converting received 10 bit value to mV (3.3*1000*i/p /1023)
28         x = adc(7);
29         adc_data = (unsigned int)(x * 3.2258)*5.05;
30
31         // Display "Volt: " on first line of lcd
32         lcd_cmd(0x80);
33         lcd_write_string(display_msg1);
34
35         // Converting integer to string of ascii
36         int_to_string(adc_data, adc_ip_data_ascii);
37
38         // Print analog sampled input on lcd in the format "XXXXXX mV"
39         lcd_write_string(adc_ip_data_ascii);
40         lcd_write_string(display_msg2);
41     }
42 }
43

```



## 7 Final Testing

All three subsystems were then integrated on a breadboard and tested together. The testing worked and voltages in the range of 12V-15V were obtained from a 5V supply.

We have performed load testing for 1.2k  $\Omega$  and 10k  $\Omega$  resistances and observed the appropriate current values. It was observed that the output voltage did not change with the change in the load resistance.

**Link:** Click for final open circuit testing video

**Link:** Click for load testing video

### 7.1 Code for the full system

```
1  /*****
2  This is the final code that integrates all the subsystems (digipot,
   adc, lcd, and switches to the PMIC)
3  *****/
4
5  #include <at89c5131.h>
6  #include "digipot.h"
7  #include "spi.h"
8  #include "lcd.h"
9  #include "adc.h"
10
11 int resis;
12 int min_bit;
13 int max_bit;
14
15 // Setting the default, min and max resistance respectively
16 unsigned long int def_resistance = 500;
17 unsigned long int low_res = 100;
18 unsigned long int high_res = 35000;
19
20 int j = 0;
21 unsigned int adc_data = 0;
22
23 code unsigned char display_msg1[] = "Fine inc ";
24 code unsigned char display_msg2[] = "Fine dec ";
25 code unsigned char display_msg3[] = "Course inc ";
26 code unsigned char display_msg4[] = "Course dec ";
27 code unsigned char display_msg5[] = "Hit minimum ";
28 code unsigned char display_msg6[] = "Hit maximum ";
29
30 code unsigned char display_txt1[] = "Volt.: ";
31 code unsigned char display_txt2[] = " mV";
32
33 char data_ascii[6] = {0, 0, 0, 0, 0, '\0'};
34 char bit_ascii[6] = {0, 0, 0, 0, 0, '\0'};
35
36 //Specifying the pins for the input switches
```

```

37 sbit inc = P3^4;
38 sbit dec = P3^5;
39 sbit mode = P3^6;
40
41 void main(void){
42
43     digipot_init();
44     spi_init();
45     lcd_init();
46     adc_init();
47
48     mode = 0;
49     inc = 0;
50     dec = 0;
51
52     resis = def_resistance*256/100000;
53     min_bit = low_res*256/100000;
54     max_bit = high_res*256/100000;
55
56     // Loop to update the value of the digipot and obtain the required
57     // voltage according to the inputs given
58     while(1){
59         //collecting the value from adc
60         unsigned int x;
61         x = adc(7);
62         adc_data = (unsigned int)((x * 3.2258 * 4.95) - 0.13);
63
64         msdelay(100);
65         int_to_string(resis,bit_ascii);
66
67         lcd_cmd(0x80) ;
68
69         //Now checking for updates
70         //first line prints the voltage
71         //second line prints the resis bit
72
73         if(mode == 1){//fine control
74
75             if(inc == 1 && dec == 0){//fine increase
76                 resis += 1;
77                 lcd_cmd(0x01);
78                 lcd_write_string(display_txt1);
79                 int_to_string(adc_data, data_ascii);
80                 lcd_write_string(data_ascii);
81                 lcd_write_string(display_txt2);
82                 lcd_cmd(0xC0);
83                 lcd_write_string(display_msg1);
84                 lcd_write_string(bit_ascii);
85                 msdelay(100);
86             }
87             else if(inc == 0 && dec == 1){//fine decrease
88                 resis -= 1;
89                 lcd_cmd(0x01);
90                 lcd_write_string(display_txt1);

```

```

90         int_to_string(adc_data, data_ascii);
91         lcd_write_string(data_ascii);
92         lcd_write_string(display_txt2);
93         lcd_cmd(0xC0);
94         lcd_write_string(display_msg2);
95         lcd_write_string(bit_ascii);
96         msdelay(100);
97     }
98 }
99 else if(mode == 0) { //course control
100
101     if(inc == 1 && dec == 0){ //course increase
102         resis += 5;
103         lcd_cmd(0x01);
104         lcd_write_string(display_txt1);
105         int_to_string(adc_data, data_ascii);
106         lcd_write_string(data_ascii);
107         lcd_write_string(display_txt2);
108         lcd_cmd(0xC0);
109         lcd_write_string(display_msg3);
110         lcd_write_string(bit_ascii);
111         msdelay(100);
112     }
113     else if(inc == 0 && dec == 1){ //course decrease
114         resis -= 5;
115         lcd_cmd(0x01);
116         lcd_write_string(display_txt1);
117         int_to_string(adc_data, data_ascii);
118         lcd_write_string(data_ascii);
119         lcd_write_string(display_txt2);
120         lcd_cmd(0xC0);
121         lcd_write_string(display_msg4);
122         lcd_write_string(bit_ascii);
123         msdelay(100);
124     }
125 }
126
127 if(resis < min_bit){ // Checking for the min limit
128     resis = min_bit;
129     lcd_cmd(0x01);
130     lcd_write_string(display_txt1);
131     int_to_string(adc_data, data_ascii);
132     lcd_write_string(data_ascii);
133     lcd_write_string(display_txt2);
134     lcd_cmd(0xC0);
135     lcd_write_string(display_msg5);
136     lcd_write_string(bit_ascii);
137     msdelay(100);
138 }
139 else if(resis > max_bit){ // Checking for the max limit
140     resis = max_bit;
141     lcd_cmd(0x01);
142     lcd_write_string(display_txt1);
143     int_to_string(adc_data, data_ascii);

```

```
144     lcd_write_string(data_ascii);
145     lcd_write_string(display_txt2);
146     lcd_cmd(0xC0);
147     lcd_write_string(display_msg6);
148     lcd_write_string(bit_ascii);
149     msdelay(100);
150 }
151 digipot_write(resis); // Writing the value of resis to digipot
152 }
153 }
```

## 8 Components BOM

Table 1: Components Used

| S. No | Component          | Specification  | Quantity | Price (INR p.u.) |
|-------|--------------------|--|----------|------------------|
| 1     | Microcontroller    | pt-51 (WEL Lab)  | 1        | 250              |
| 2     | Digipot            | MCP4161  | 1        | 120              |
| 3     | PMIC (boost)       | LMR62421   | 1        | 130              |
| 4     | PMIC (boost)       | TPS61040DBVR (backup)  | 1        | 134              |
| 5     | Schottky Diode     | SR150  | 1        | 2.4              |
| 6     | USB Type C         | Breakout Pcb Board Pins  | 1        | 100              |
| 7     | Push Button Switch | R13-507  | 2        | 21               |
| 8     | Rocker Switch      | SPST   | 1        | 16.4             |
| 9     | Resistance         | 8.2 k $\Omega$ , 1 M $\Omega$ , 6.2 k $\Omega$ , 22 k $\Omega$ | 4        | WEL              |
| 10    | Inductor           | 16uH   | 1        | WEL              |
| 11    | Capacitor          | 22 uF, 4.7 uF, 470 pF, 0.1 uF                                  | 4        | WEL              |
| 12    | ADC                | MCP3008  | 1        | 198              |

## 9 Major Problems Faced

| S No. | Problems   | Solution  |
|-------|--|---|
| 1     | The previous ADC, MAX1118 used 3 wire SPI and hence required additional pins for implementation. We weren't able to achieve the exact timing diagram for CNVST, clock, data input which lead to improper transmission of data. | We switched to MCP3008, a 10-bit ADC available in WEL, which supported direct SPI connection  |
| 2     | The previous digipot, MAX5401 had a similar SPI interfacing issue. Hence went into wiper default mode and the digipot no longer updated the wiper positions.   | We switched to MCP4161, 100k digipot available in lab and were able to successfully integrate that.   |
| 3     | For the current digipot MCP4161, the maximum voltage allowed across its pins was 3.6 V; otherwise it would go into WiperLock protection mode and disable the SPI communication.  | To ensure this did not happen in our range of output voltages, we added a resistance in series with the digipot to keep the digipot resistance smaller and therefore, reduce the voltage across it. |

## 10 Future Work

Currently, we have successfully implemented the project on a breadboard. The efficiency would be higher when implemented on a PCB because of lesser wiring, loose connections and other such errors. The power supply could be improved by adding voltage regulators based on the end application, to avoid any abrupt increase or decrease in voltage which could damage components. Fuses can also be used as a mitigation strategy. More extensive load testing can also be performed to see if the miniature programmable power supply is capable of giving load currents as high as 0.2 A.